
 


Homework #5

 1. Using sequential circuit design procedure beginning with a state diagram, convert a D-type flip-flop to a T-type flip-flop by adding input logic. Show that the logic obtained is an exclusive-OR gate..



Present State	Inputs	Next State
$Q(t)$	T	$D(t)$
0	0	0
0	1	1
1	0	1
1	1	0




$$D = \bar{Q} \cdot T + Q \cdot \bar{T}$$

This is the definition of an exclusive or gate!

2. Implement the following Boolean function with an 8-to-1 line multiplexer and a single inverter:


$$F(A, B, C, D) = \sum m(2,3,5,6,8,9,12,14)$$

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

 


3. Design a sequential circuit using two D flip-flops A and B and combinational logic. Your circuit has one input X and one output Y, and is defined by the following state diagram — Traditional Design Solution


Present State		Inputs X	Next State		Output Y
$Q_1(t)$	$Q_0(t)$		$D_0(t)$	$D_1(t)$	
0	0	0	0	1	1
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	0	0	0
1	1	0	1	0	0
1	1	1	1	1	0

 

$$D_1 = Q_0X + Q_1\bar{X}$$

 

 
$$D_0 = Q_0 \cdot X + \bar{Q}_1 \cdot \bar{X}$$



$$Y = \bar{Q}_1 \cdot \bar{Q}_0$$

 4. A sequential circuit has two flip-flops A and B, one input X and one output Y. The state diagram is shown below. Design the circuit with D flip-flops. — Design using One-Hot State Encoding



$$S0(t+1) = D0(t) = X \cdot S0 + X \cdot S2 = X(Q0 + Q2)$$


$$S1(t+1) = D1(t) = \bar{X} \cdot S0 + \bar{X} \cdot S1 = \bar{X}(Q0 + Q1)$$

$$S2(t+1) = D2(t) = \bar{X} \cdot S2 + \bar{X} \cdot S3 = \bar{X}(Q2 + Q3)$$

$$S3(t+1) = D3(t) = X \cdot S1 + X \cdot S3 = X(Q1 + Q3)$$

$$Y(t) = S0(t) = Q0$$

 5. Convert a D-type flip-flop into a JK flip-flop, using external gates. The gates can be derived by means of a sequential circuit design procedure starting from a state table with the D flip-flop output as the present state and its input as the next state and with J and K as circuit inputs.



Present State	Inputs		Next State
	$Q(t)$	J	
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

D

		JK			
		00	01	11	10
Q	0			1	1
	1	1			1
		K			

$$D = \bar{Q}J + Q\bar{K}$$